

EE 357 Unit 2a

Multiplication Techniques

Learning Objectives

- Perform by hand the different methods for unsigned and signed multiplication
- Understand the various digital implementations of a multiplier along with their tradeoffs
 - Sequential add and shift method
 - Basic combinational array multiplier
 - Booth and/or Bit-Pair multiplier

Add and Shift Method (Sequential)
Booth's Coding and Bit-Pair Recoding

MULTIPLICATION TECHNIQUES

Unsigned Multiplication Review

- Same rules as decimal multiplication
- Multiply each bit of Q by M shifting as you go
- An m-bit * n-bit mult. produces an m+n bit result (i.e. n-bit * n-bit produces 2*n bit result)
- Notice each partial product is a shifted copy of M or 0 (zero)



	1010	M (Multiplicand)
*	1011	Q (Multiplier)
	<hr/>	
	1010	
	1010_	PP (Partial
	0000_	Products)
	<hr/>	
+	1010	
	<hr/>	
	01101110	P (Product)

Multiplication Techniques

- A multiplier unit can be
 - Purely Combinational: Each partial product is produced in parallel and fed into an array of adders to generate the product
 - Sequential and Combinational: Produce and add 1 partial product at a time (per cycle)

Combinational Multiplier

  - Partial Product (PP_i) Generation
 - Multiply $Q[i] * M$
 - if $Q[i]=0 \Rightarrow PP_i = 0$
 - if $Q[i]=1 \Rightarrow PP_i = M$
 - AND gates can be used to generate each partial product




Combinational Multiplier

- Partial Products must be added together
- Combinational multipliers suffer from long propagation delay through the adders
 - propagation delay is proportional to the number of partial products (i.e. number of bits of input) and the width of each adder


Adder Propagation Delay
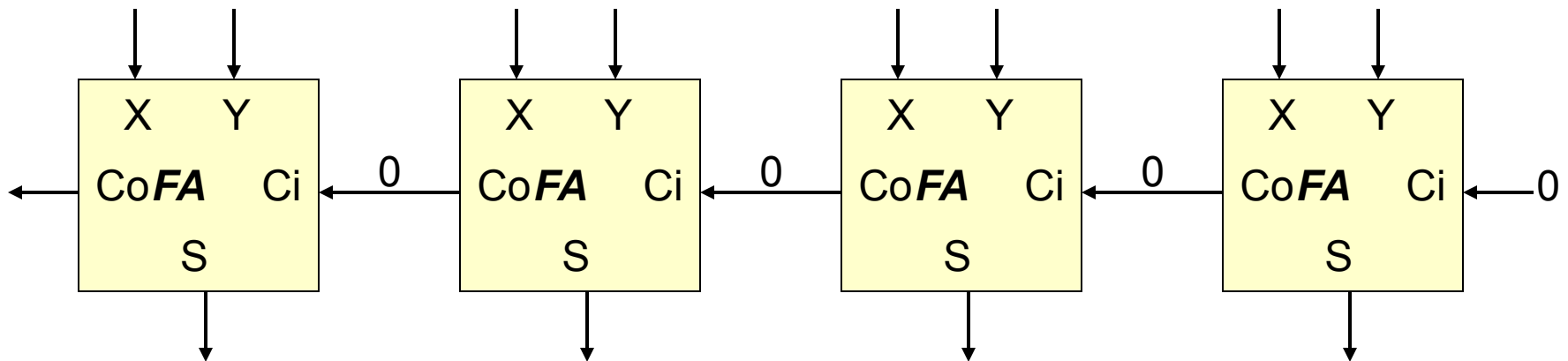
$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$




Adder Propagation Delay
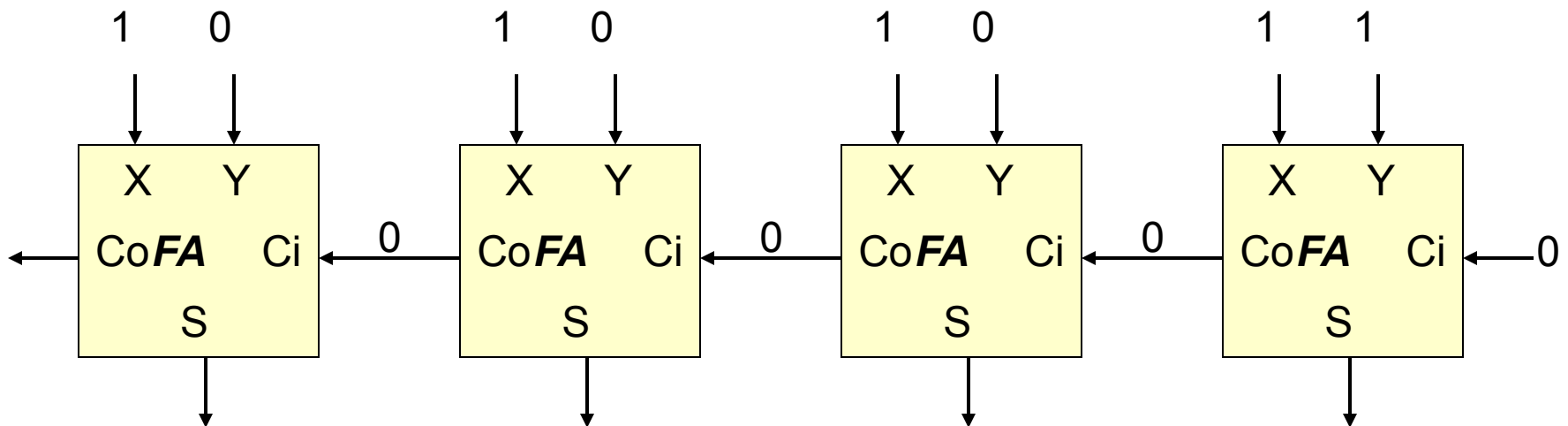
$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$




Adder Propagation Delay
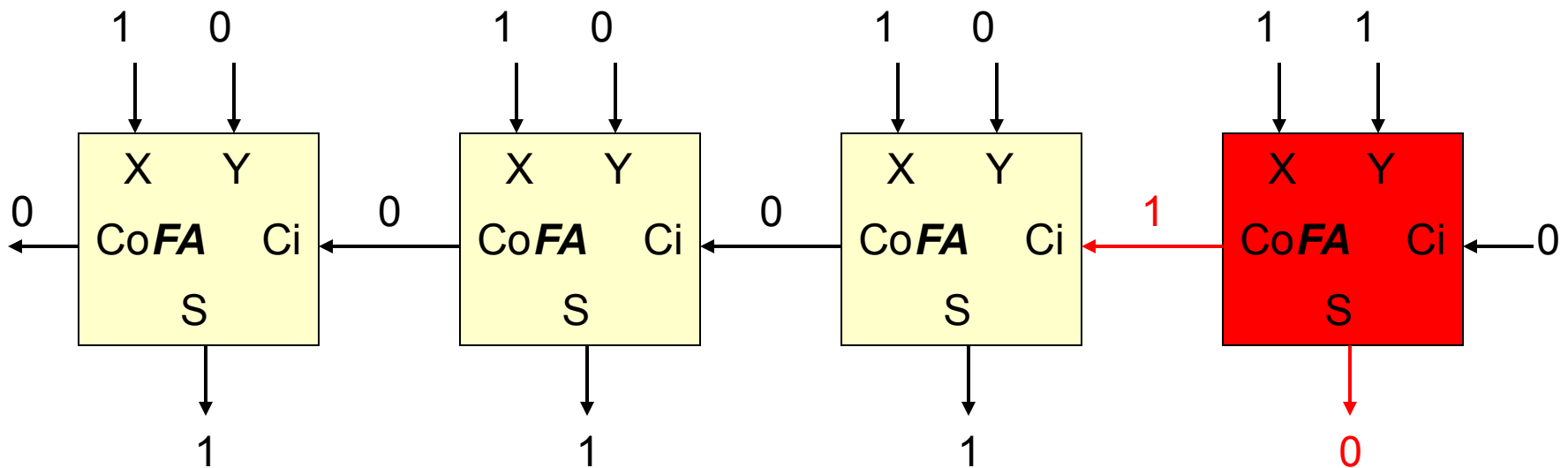
$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$




Adder Propagation Delay
 
$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$




Adder Propagation Delay
 
$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$



Adder Propagation Delay
 
$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$




Critical Path

- Critical Path = Longest possible delay path


Assume $t_{\text{sum}} = 5 \text{ ns}$,

$t_{\text{carry}} = 4 \text{ ns}$

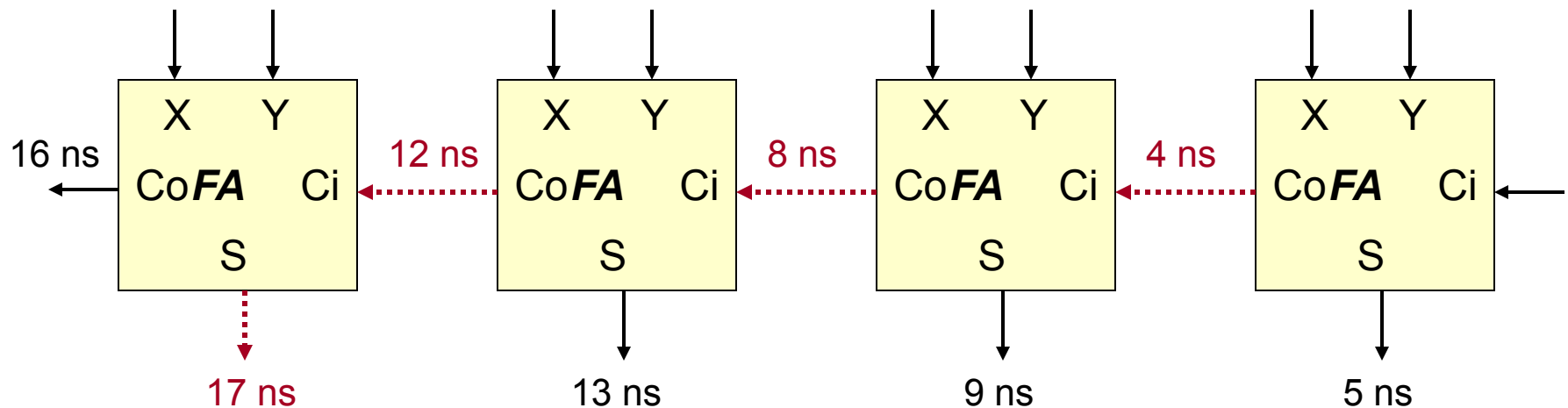


←..... Critical Path


Combinational Multiplier

 


Combinational Multiplier

 


Combinational Multiplier

 


Combinational Multiplier

 


Combinational Multiplier

 


Combinational Multiplier

 


Combinational Multiplier

 


Combinational Multiplier

 

Combinational Multiplier

 

Critical Paths

 

←..... Critical Path 1

←..... Critical Path 2

Combinational Multiplier Analysis

- Large Area due to $(n-1)$ m-bit adders
 - $n-1$ because the first adder adds the first two partial products and then each adder afterwards adds one more partial product
- Propagation delay is in two dimensions
 - proportional to $m+n$

Sequential Multiplier

- Use 1 adder to add a single partial product per clock cycle keeping a running sum

Add and Shift Method

- Sequential algorithm
- n -bit * n -bit multiply
- Adds 1 partial product per clock
- Shift running sum 1-bit right each clock
- Three n -bit Registers, 1 Adder
- At start:
 - M = Multiplicand
 - Q = Multiplier
 - A = Answer \Rightarrow initialized to 0
- After completion
 - A and Q concatenate to form $2n$ -bit answer

$$\begin{array}{rcl} & 1010 & = \text{M} \\ * & 1011 & = \text{Q} \\ \hline \end{array}$$

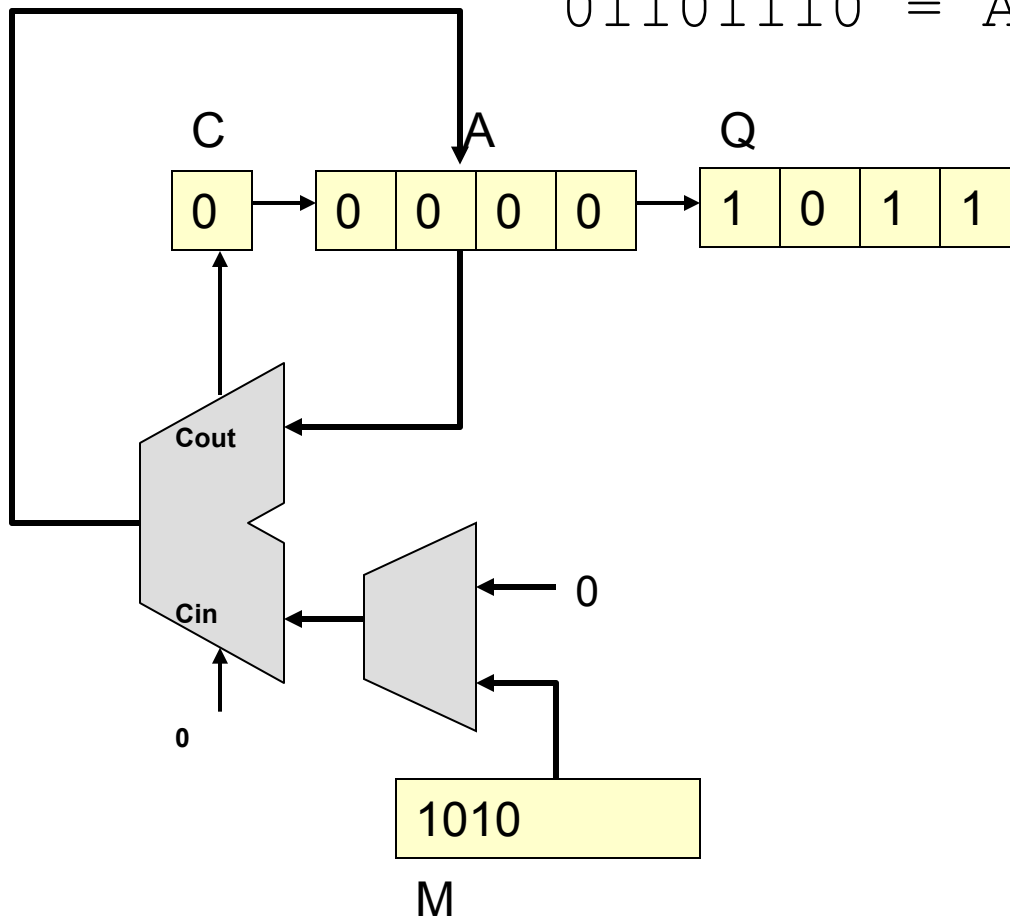

Add and Shift Algorithm

- $C=0, A=0$
- Repeat the following n-times
 - If $Q[0] = 0$, $A = A+0$
Else if $Q[0] = 1$, $A = A+M$
 - Shift right 1-bit ($0 \rightarrow C \rightarrow A \rightarrow Q$)

$$\begin{array}{r} 1010 \\ * 1011 \\ \hline \end{array}$$

Add and Shift Multiplication

$$\begin{array}{r}
 1010 = M \\
 * 1011 = Q \\
 \hline
 01101110 = \text{Ans}
 \end{array}$$




M = 1010

C	A	Q
0	0000	1011

Add and Shift Multiplication

$$\begin{array}{r}
 1010 = M \\
 * 1011 = Q \\
 \hline
 01101110 = \text{Ans}
 \end{array}$$
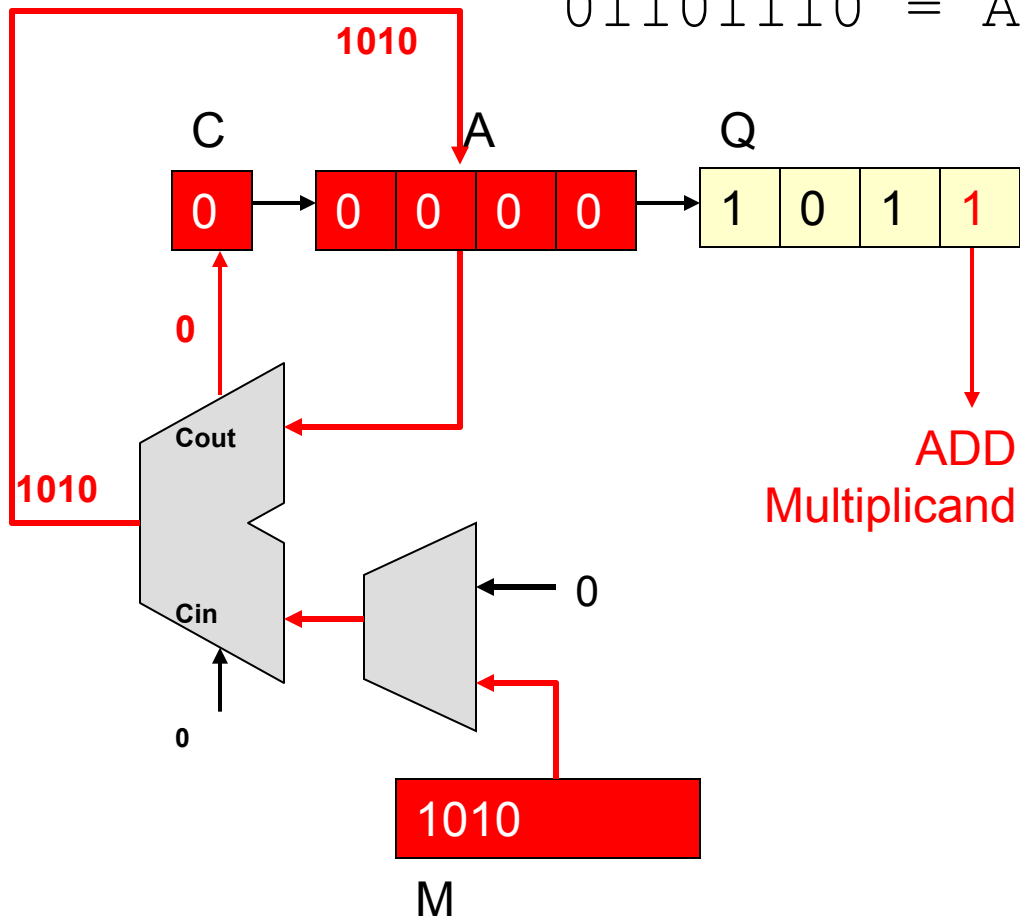
$$\begin{array}{r}
 1010 \\
 * 1011 \\
 \hline
 + 1010 \\
 \hline
 1010
 \end{array}$$




ADD
Multiplicand

M = 1010		
C	A	Q
0	0000	1011
0	1010	1011


→ Add

$$\begin{array}{rcl} & 1010 & = M \\ * & 1011 & = Q \\ \hline 01101110 & = & \text{Ans} \end{array}$$
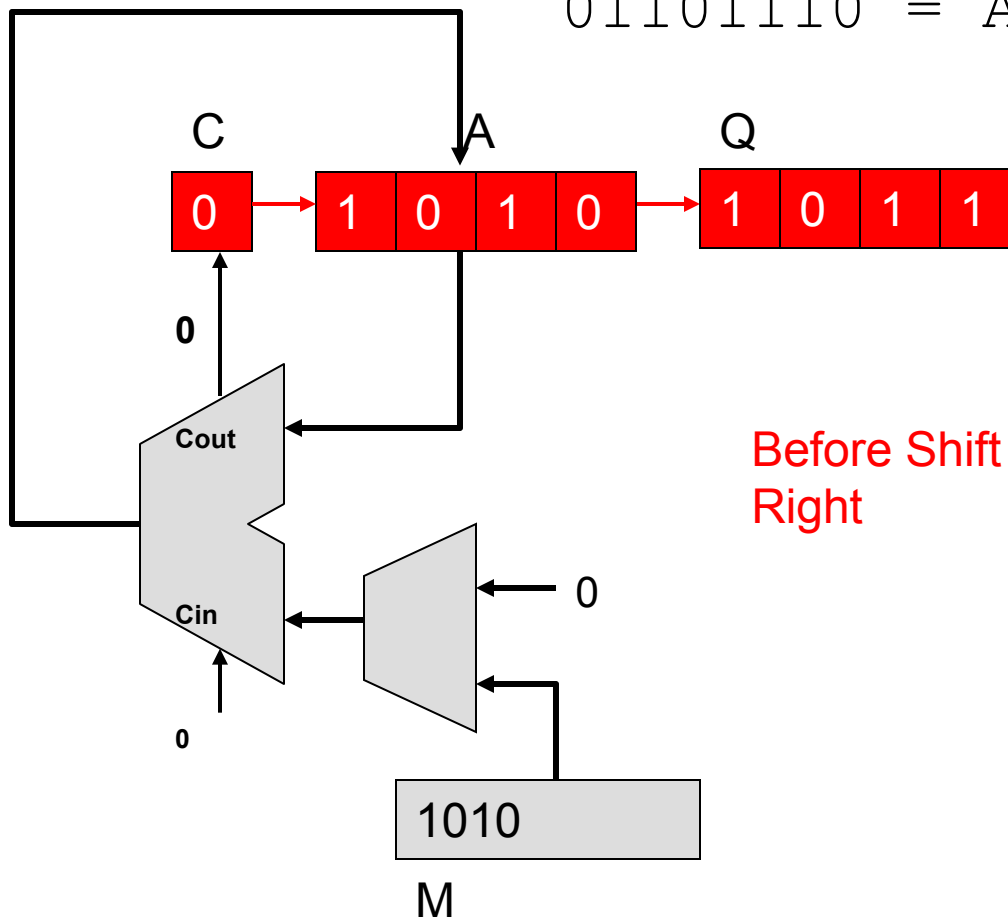
$$\begin{array}{r} 1010 \\ * 1011 \\ \hline + 1010 \\ \hline 1010 \end{array}$$





Before Shift
Right


 


Add and Shift Multiplication

$$\begin{array}{r}
 1010 = M \\
 * 1011 = Q \\
 \hline
 01101110 = \text{Ans}
 \end{array}$$
 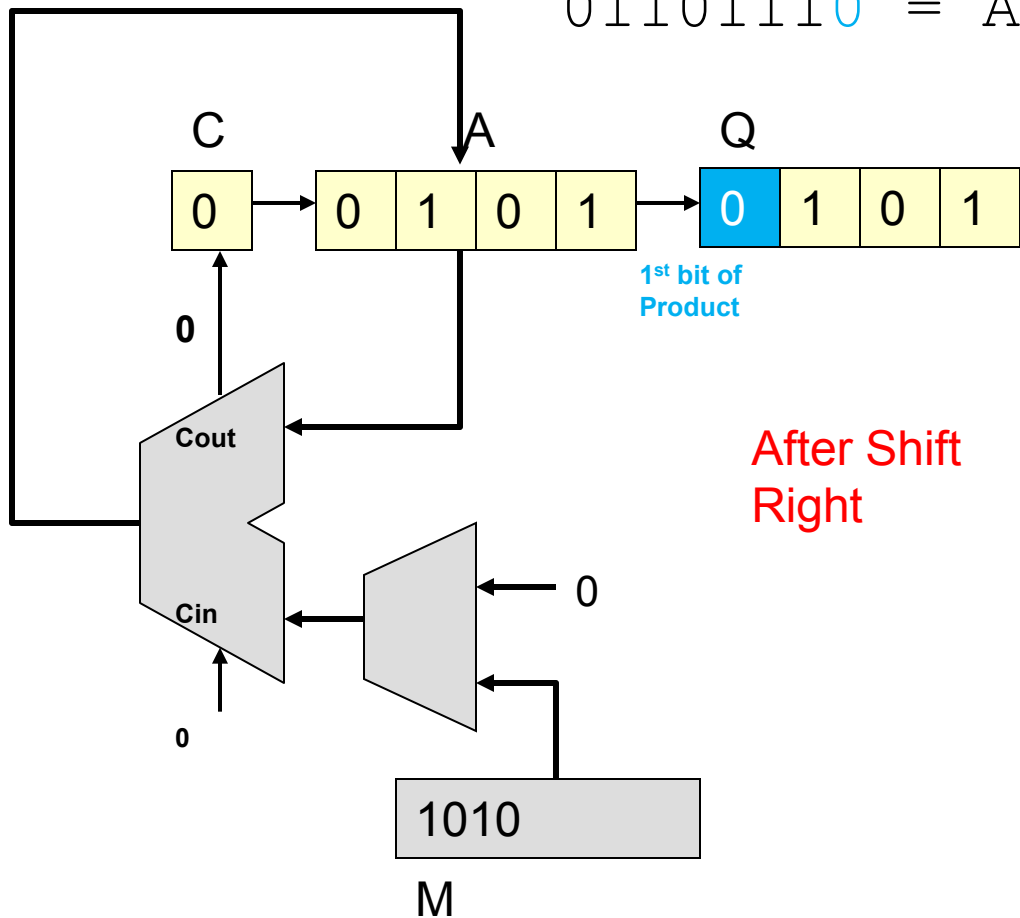
$$\begin{array}{r}
 1010 \\
 * 1011 \\
 \hline
 + 1010 \\
 \hline
 1010
 \end{array}$$




  
$$\begin{array}{rcl} & 1010 & = M \\ * & 1011 & = Q \\ \hline 01101110 & = & \text{Ans} \end{array}$$


Add and Shift Multiplication

$$\begin{array}{r}
 1010 = M \\
 * 1011 = Q \\
 \hline
 01101110 = \text{Ans}
 \end{array}$$

 
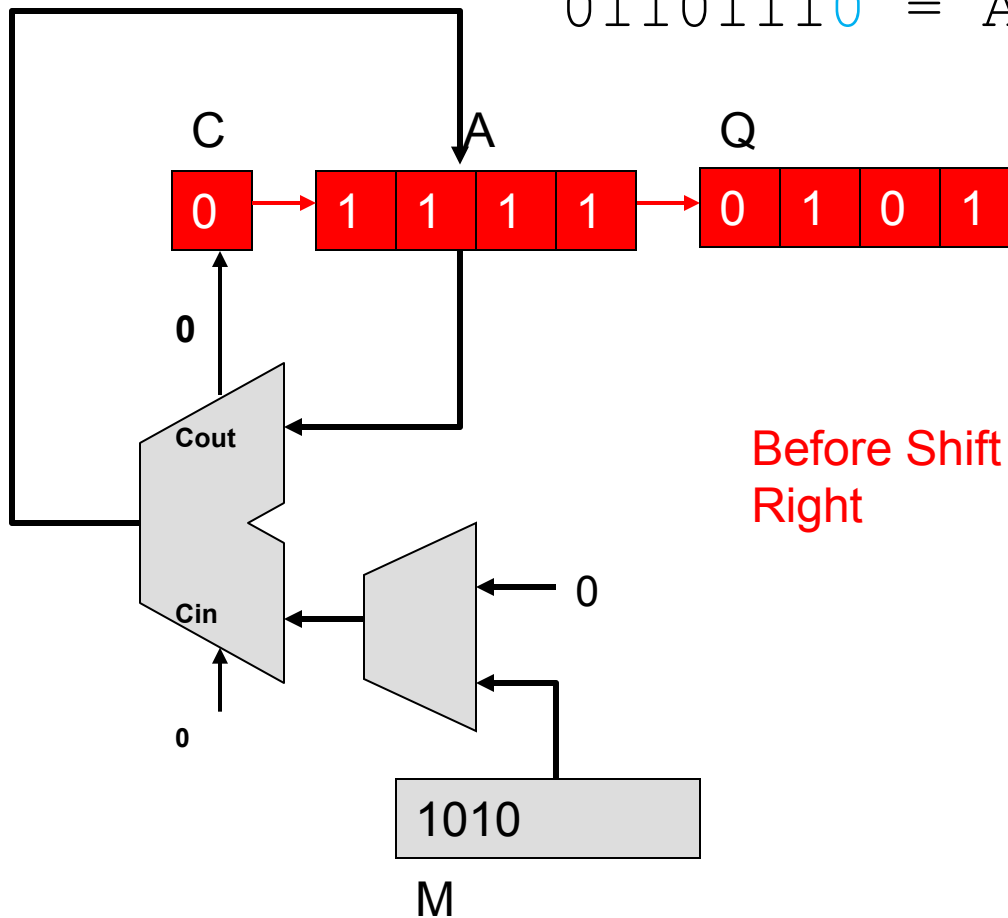
$$\begin{array}{r}
 1010 \\
 * 1011 \\
 \hline
 1010 \\
 1010 \\
 + 1010 - \\
 \hline
 011110
 \end{array}$$





Add and Shift Multiplication

$$\begin{array}{r}
 1010 = M \\
 * 1011 = Q \\
 \hline
 01101110 = \text{Ans}
 \end{array}$$
 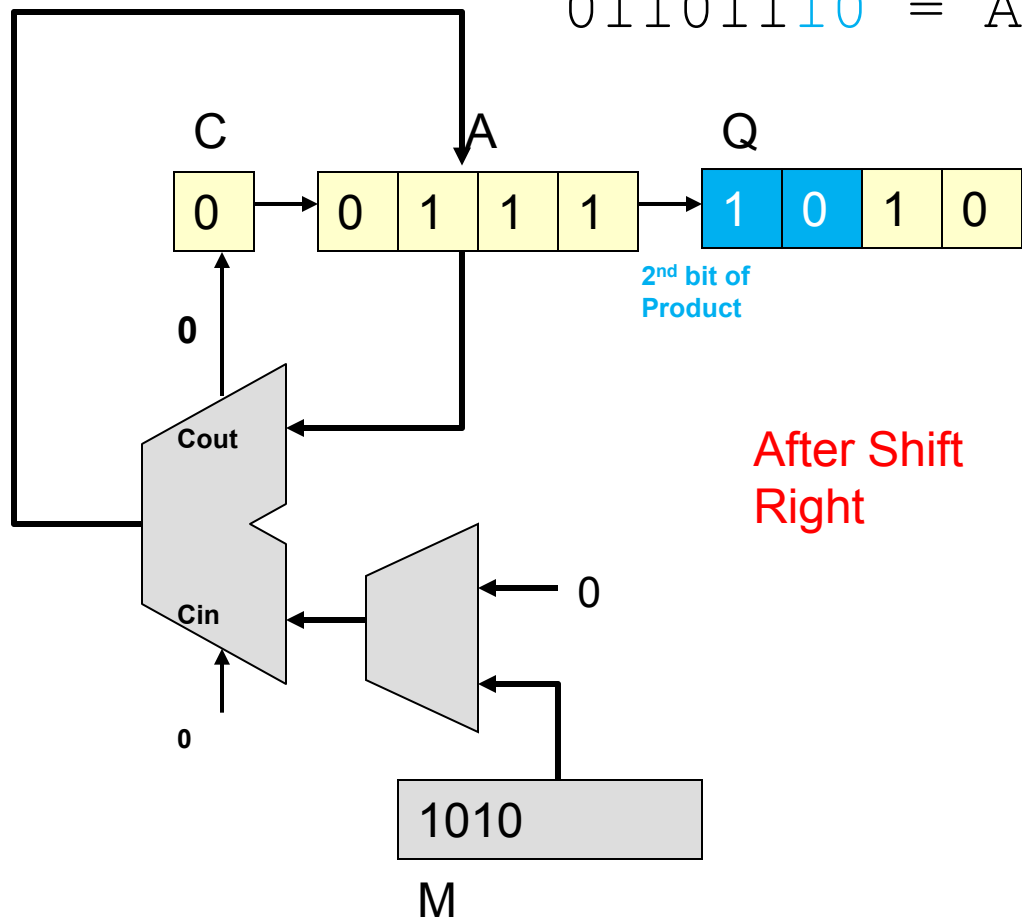
$$\begin{array}{r}
 1010 \\
 * 1011 \\
 \hline
 1010 \\
 1010 \\
 + 1010 - \\
 \hline
 011110
 \end{array}$$



  
$$\begin{array}{rcl} & 1010 & = M \\ * & 1011 & = Q \\ \hline 01101110 & = & \text{Ans} \end{array}$$


Add and Shift Multiplication

$$\begin{array}{r} 1010 = M \\ * 1011 = Q \\ \hline 01101110 = \text{Ans} \end{array}$$
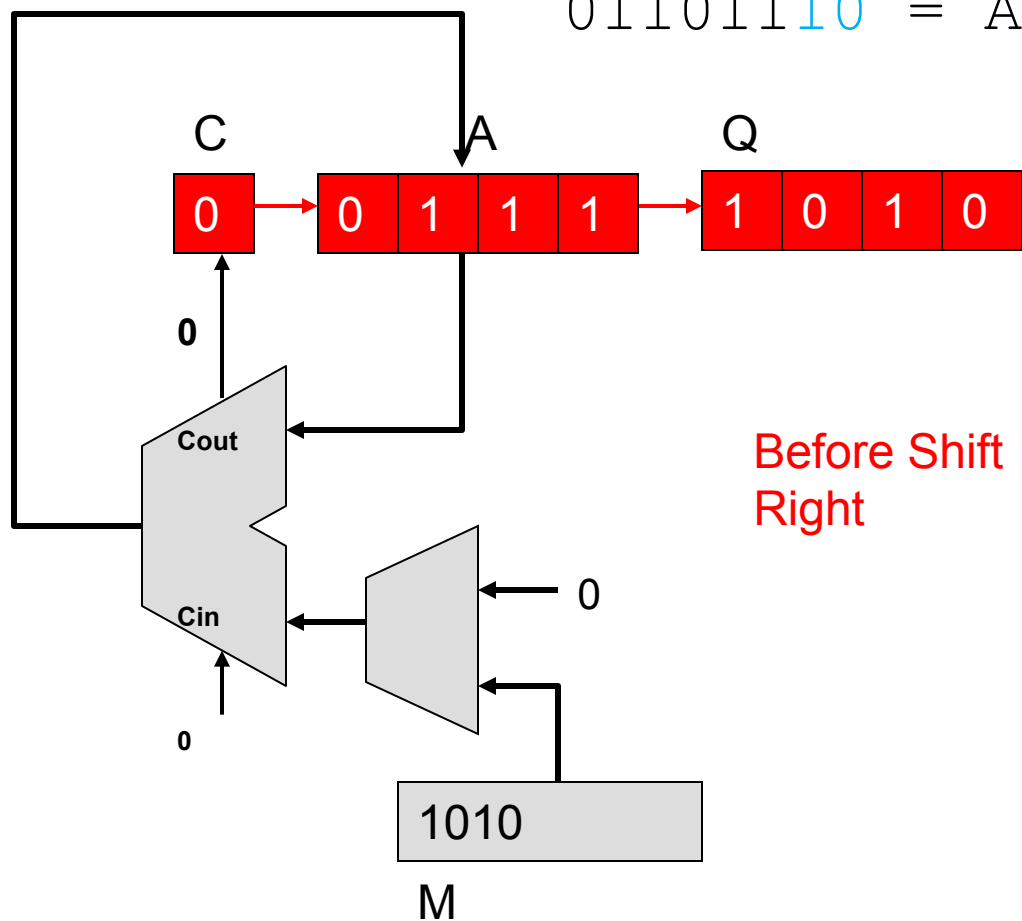
$$\begin{array}{r} 1010 \\ * 1011 \\ \hline + 1010 \\ \hline 1010 \\ + 1010 - \\ \hline 011110 \\ + 0000 - - \\ \hline 0011110 \end{array}$$




M = 1010			
C	A	Q	
0	0000	1011	
0	1010	1011	Add Shift
0	0101	0101	Add Shift
0	1111	0101	Add Shift
0	0111	1010	No Add Shift
0	0011	1101	

Add and Shift Multiplication

$$\begin{array}{r} 1010 = M \\ * 1011 = Q \\ \hline 01101110 = \text{Ans} \end{array}$$
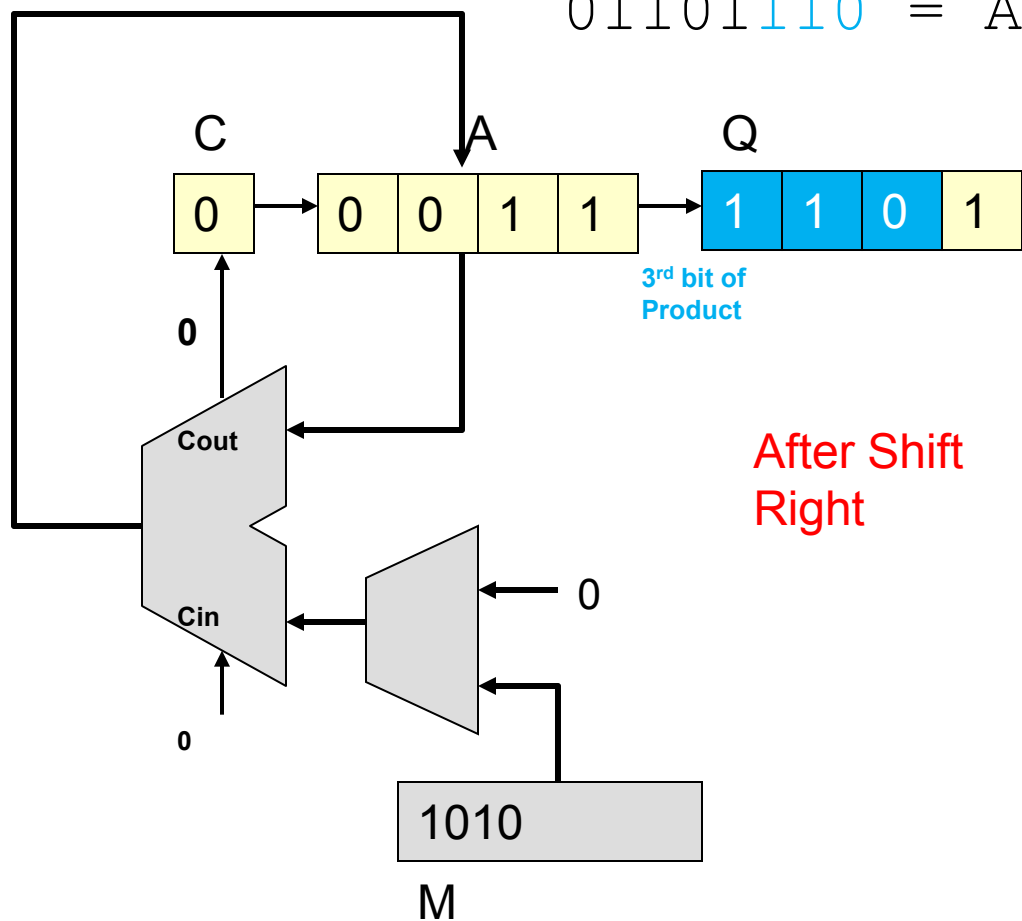
$$\begin{array}{r} 1010 \\ * 1011 \\ \hline + 1010 \\ \hline 1010 \\ + 1010- \\ \hline 011110 \\ + 0000-- \\ \hline 0011110 \end{array}$$




After Shift
Right

M = 1010			
C	A	Q	
0	0000	1011	
0	1010	1011	Add Shift
0	0101	0101	
0	1111	0101	Add Shift
0	0111	1010	
0	0111	1010	No Add Shift
0	0011	1101	

Add and Shift Multiplication
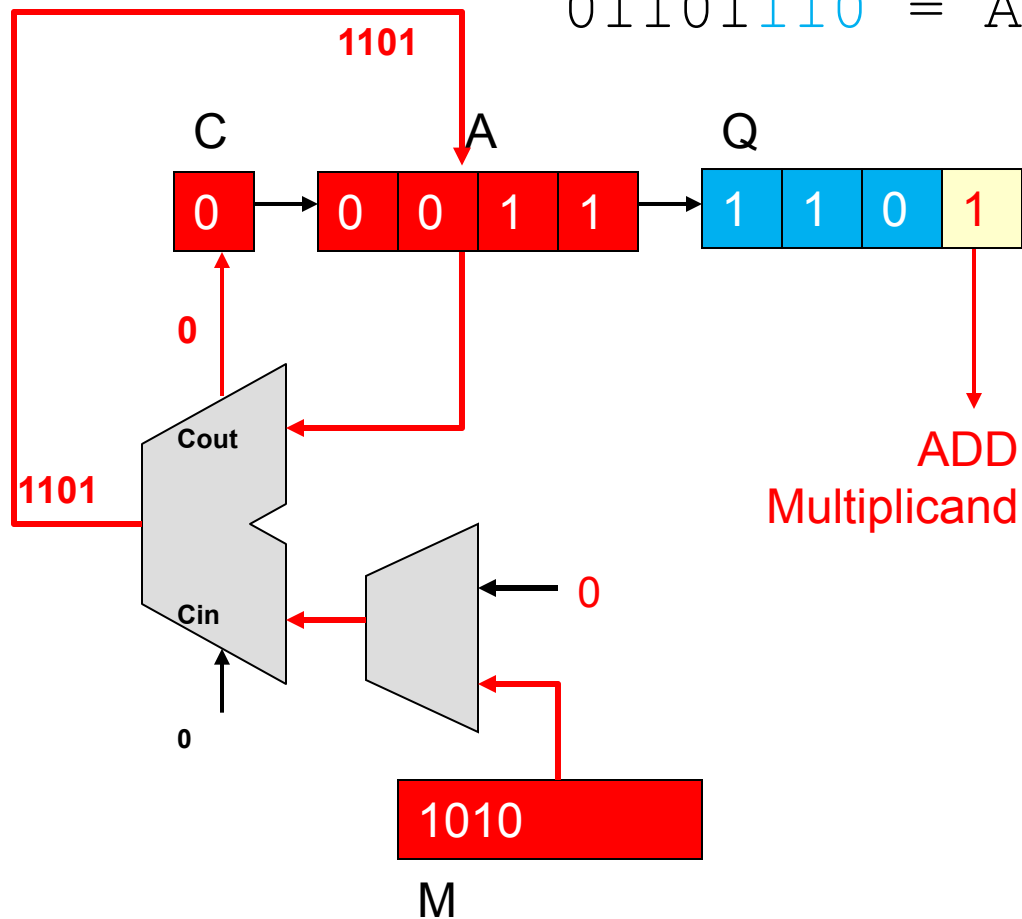
$$\begin{array}{r}
 1010 = M \\
 * 1011 = Q \\
 \hline
 01101110 = \text{Ans}
 \end{array}$$



$$\begin{array}{r}
 1010 \\
 * 1011 \\
 \hline
 + 1010 \\
 \hline
 1010 \\
 + 1010 - \\
 \hline
 011110 \\
 + 0000 - - \\
 \hline
 0011110 \\
 + 1010 - - - \\
 \hline
 01101110
 \end{array}$$

M = 1010			
C	A	Q	
0	0000	1011	
0	1010	1011	Add
0	0101	0101	Shift
0	1111	0101	Add
0	0111	1010	Shift
0	0111	1010	No Add
0	0011	1101	Shift
0	1101	1101	Add

$$\begin{array}{rcl} & 1010 & = M \\ * & 1011 & = Q \\ \hline 01101110 & = & \text{Ans} \end{array}$$

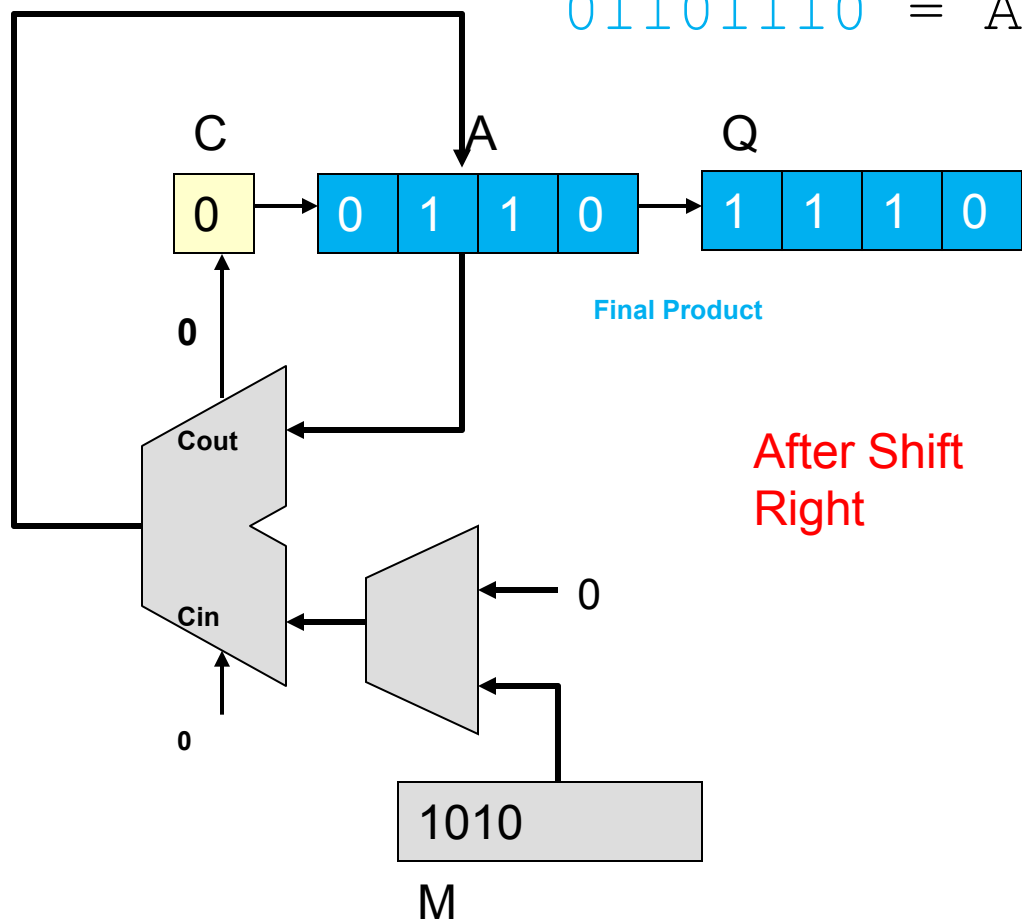

$$\begin{array}{r}
 1010 \\
 * 1011 \\
 \hline
 + 1010 \\
 \hline
 1010 \\
 + 1010 - \\
 \hline
 011110 \\
 + 0000 -- \\
 \hline
 0011110 \\
 + 1010 --- \\
 \hline
 01101110
 \end{array}$$

M = 1010

C	A	Q	Operation
0	0000	1011	
0	1010	1011	Add Shift
0	0101	1011	Add Shift
0	1111	1011	Add Shift
0	0111	1011	Add Shift
0	0111	1010	No Add Shift
0	1101	1101	Add Shift
0	0110	1101	Add Shift

Add and Shift Multiplication

$$\begin{array}{r} 1010 = M \\ * 1011 = Q \\ \hline 01101110 = \text{Ans} \end{array}$$




$$\begin{array}{r} 1010 \\ * 1011 \\ \hline + 1010 \\ \hline 1010 \\ + 1010 - \\ \hline 011110 \\ + 0000 -- \\ \hline 0011110 \\ + 1010 --- \\ \hline 01101110 \end{array}$$

M = 1010			
C	A	Q	
0	0000	1011	
0	1010	1011	Add Shift
0	0101	0101	Add Shift
0	1111	0101	Add Shift
0	0111	1010	No Add Shift
0	0011	1101	No Add Shift
0	1101	1101	Add Shift
0	0110	1110	Add Shift

Add and Shift Multiplication

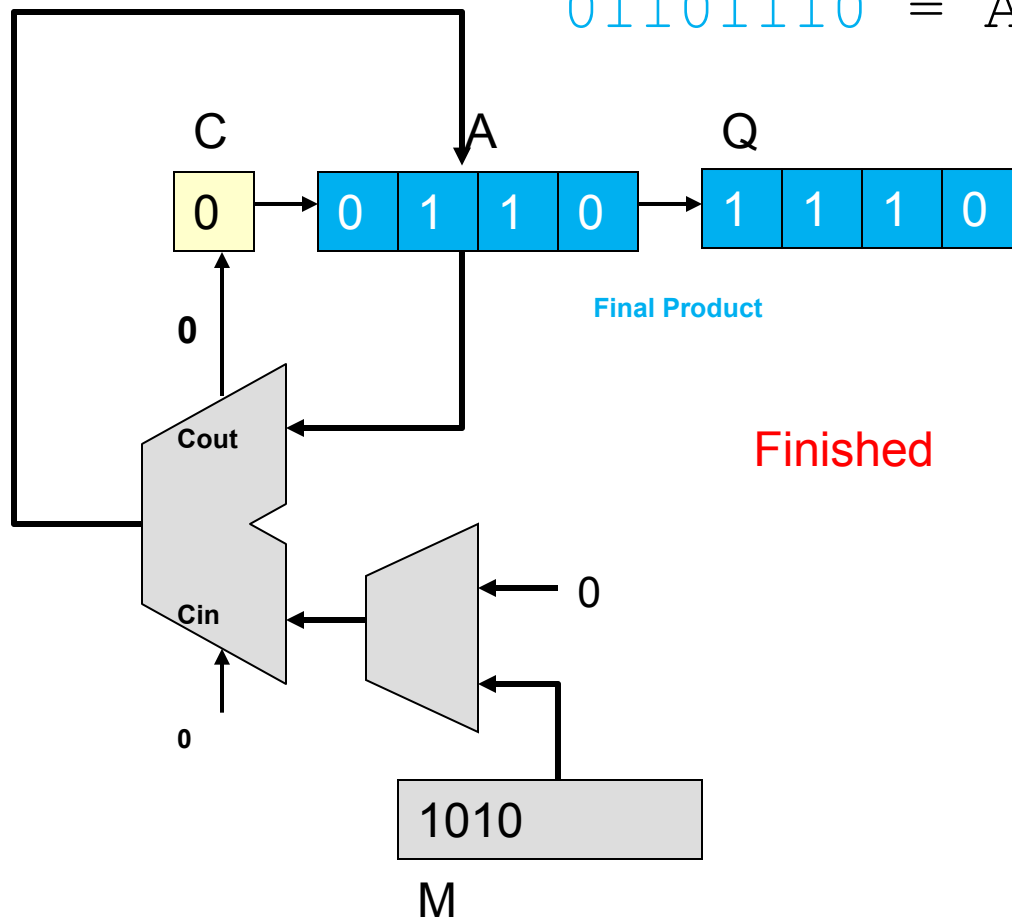
$$\begin{array}{r} 1010 = M \\ * 1011 = Q \\ \hline 01101110 = \text{Ans} \end{array}$$



$$\begin{array}{r} 1010 \\ * 1011 \\ \hline + 1010 \\ \hline 1010 \\ + 1010- \\ \hline 011110 \\ + 0000-- \\ \hline 0011110 \\ + 1010--- \\ \hline 01101110 \end{array}$$

M = 1010			
C	A	Q	
0	0000	1011	
0	1010	1011	Add
0	0101	0101	Shift
0	1111	0101	Add
0	0111	1010	Shift
0	0111	1010	No Add
0	0011	1101	Shift
0	1101	1101	Add
0	0110	1110	Shift
	0110	1110	= 110 ₁₀

1101 * 0101 Example

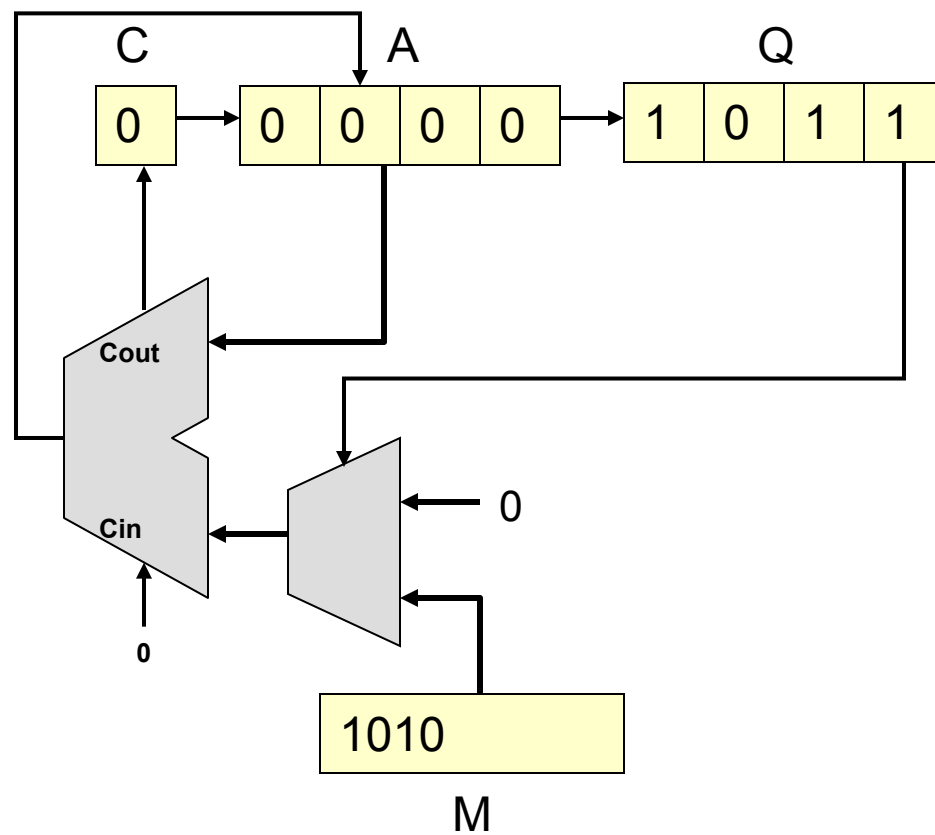

C=	M=1101 A=0000	Q=0101	Description
0	1101	0101	A=A+M
0	0110	1010	Shift Right C,A,Q
0	0110	1010	A=A+0
0	0011	0101	Shift Right C,A,Q
1	0000	0101	A=A+M
0	1000	0010	Shift Right C,A,Q
0	1000	0010	A=A+0
0	0100	0001	Shift Right C,A,Q

Sequential Multiplier Analysis

- Pros:
 - Smaller Area due to the use of only 1 adder
- Cons:
 - Slow to execute (2 cycles per bit of the multiplier)

Multipliers

- Most multipliers are combinational
 - Faster than sequential method
- To increase speed
 - Make faster adders
 - Reduce # of additions (i.e. # of partial products)...See Bit Pair Recoding later in this lecture

Signed Multiplication Techniques

- When adding signed (2's comp.) numbers, some new issues arise
- Must sign extend partial products (out to 2n bits)

**Without Sign Extension...
Wrong Answer!**

$$\begin{array}{r}
 1001 = -7 \\
 * 0110 = +6 \\
 \hline
 0000 \\
 1001\text{ }_ \\
 1001\text{ }_ \\
 + 0000 \\
 \hline
 00110110 = +54
 \end{array}$$

**With Sign Extension...
Correct Answer!**

$$\begin{array}{r}
 1001 = -7 \\
 * 0110 = +6 \\
 \hline
 00000000 \\
 1111001\text{ }_ \\
 111001\text{ }_ \\
 + 00000 \\
 \hline
 11010110 = -42
 \end{array}$$

Signed Multiplication Techniques

- Also, must worry about negative multiplier
 - MSB of multiplier has negative weight
 - If MSB=1, multiply by -1 (i.e. take 2's comp. of multiplicand)

With Sign Extension but w/o
consideration of MSB...
Wrong Answer!

$$\begin{array}{r}
 1100 = -4 \\
 * 1010 = -6 \\
 \hline
 00000000 \\
 1111100_ \\
 000000_ \\
 + 11100_ \\
 \hline
 11011000 = -40
 \end{array}$$

With Sign Extension and w/
consideration of MSB...
Correct Answer!

Place Value: -8
Multiply by -1

$$\begin{array}{r}
 1100 = -4 \\
 * 1010 = -6 \\
 \hline
 00000000 \\
 1111100_ \\
 000000_ \\
 + 00100_ \\
 \hline
 00011000 = +24
 \end{array}$$

Booth's Algorithm

- Used for signed multiplication
 - Works regardless of sign of either operand
- Forms the basis for an optimization known as bit-pair recoding
- Requires recoding of multiplier
 - 0's and 1's \rightarrow 0's, 1's, -1's
 - Must still sign extend partial products

Booth Recoding

- Recode the multiplier using the truth table below
- Start at MSB of the multiplier and work towards the LSB
 - Bit i = current bit
 - Bit $i-1$ = bit to the right of current bit

Bit i	Bit $i-1$	Booth's Value
0	0	0
1	1	0
0	1	+1
1	0	-1

Notice Booth's Value is equal to the change from bit i to bit $(i-1)$...or really $[\text{bit } i-1] - [\text{bit } i]$

Booth's Algorithm

Original Problem:

$$\begin{array}{rcccl}
 & 0 & 1 & 0 & 1 & 0 & (+10) \\
 * & 1 & 0 & 0 & 1 & 1 & (-13) \\
 \hline
 \end{array}$$

Booth's Algorithm

Original Problem:

$$\begin{array}{r}
 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\
 * \boxed{1 \ 0} \ 0 \ 1 \ 1 \quad (-13) \\
 \hline
 \end{array}$$

-1

Bit i	Bit $i-1$	Booth's Value
0	0	0
1	1	0
0	1	+1
1	0	-1

Booth's Algorithm

Original Problem:

$$\begin{array}{r}
 01010 \quad (+10) \\
 * 10011 \quad (-13) \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 -1 \quad 0 \\
 \hline
 \end{array}$$

Bit i	Bit $i-1$	Booth's Value
0	0	0
1	1	0
0	1	+1
1	0	-1

Booth's Algorithm

Original Problem:

$$\begin{array}{r}
 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\
 * \ 1 \ 0 \ 0 \ 1 \ 1 \quad (-13) \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 -1 \ 0+1 \\
 \hline
 \end{array}$$

Bit i	Bit $i-1$	Booth's Value
0	0	0
1	1	0
0	1	+1
1	0	-1

Booth's Algorithm

Original Problem:

$$\begin{array}{r}
 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\
 * \ 1 \ 0 \ 0 \ \boxed{1 \ 1} \quad (-13) \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 -1 \ 0 +1 \ 0 \\
 \hline
 \end{array}$$

Bit i	Bit $i-1$	Booth's Value
0	0	0
1	1	0
0	1	+1
1	0	-1

Booth's Algorithm

Original Problem:

$$\begin{array}{r}
 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\
 * \ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \quad (-13) \\
 \hline
 \end{array}$$

$$\begin{array}{r}
 -1 \ 0 +1 \ 0 -1 \\
 \hline
 \end{array}$$

Bit i	Bit $i-1$	Booth's Value
0	0	0
1	1	0
0	1	+1
1	0	-1

Booth's Algorithm

Original Problem:

$$\begin{array}{r}
 0 \ 1 \ 0 \ 1 \ 0 \\
 * \ 1 \ 0 \ 0 \ 1 \ 1 \\
 \hline
 \end{array}
 \begin{array}{l}
 (+10) \\
 (-13)
 \end{array}$$

$$\begin{array}{r}
 \\
 \\
 \\
 \\
 \\
 + \\
 \hline
 1 \ 1 \ 0 \ 1 \ 1 \ 1 \ 1 \ 1 \ 1 \ 0
 \end{array}
 \begin{array}{l}
 0 \ 1 \ 0 \ 1 \ 0 \\
 * \ -1 \ 0 +1 \ 0 -1 \\
 \hline
 1 \ 1 \ 0 \ 1 \ 1 \ 0 \\
 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \\
 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0 \\
 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0
 \end{array}
 \begin{array}{l}
 (+10) \\
 (-13) \\
 (-130)
 \end{array}$$

Bit i	Bit $i-1$	Booth's Value
0	0	0
1	1	0
0	1	+1
1	0	-1

Booth's Algorithm Summary

- Recode multiplier (Q) and perform multiplication
- Works for positive or negative operands

Booth's Algorithm Summary

- Recode multiplier (Q) and perform multiplication
- Works for positive or negative operands

How fast is multiplication?

Still required to add $(n-1)$ partial products

Bit-Pair Recoding

- Works on top of Booth's algorithm
- Cuts # of partial products in half
- Method
 - Group every 2 Booth encoded multiplier bits
 - Convert to: -2,-1,0,+1,+2
 - Perform multiplication

Bit Pair Recoding

Original Problem:

$$\begin{array}{r}
 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\
 * \ 1 \ 0 \ 1 \ 1 \ 1 \quad (-9) \\
 \hline
 \end{array}$$

Bit Pair Recoding

Original Problem:

$$\begin{array}{r} 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\ * \ 1 \ 0 \ 1 \ 1 \ 1 \ 0 \quad (-9) \\ \hline \end{array}$$



Booth's Algorithm

$$\begin{array}{r} 0 \ 1 \ 0 \ 1 \ 0 \\ * \ -1 \ +1 \ 0 \ 0 \ -1 \\ \hline \end{array}$$

Bit Pair Recoding

Original Problem:

$$\begin{array}{r} 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\ * \ 1 \ 0 \ 1 \ 1 \ 1 \ 0 \quad (-9) \\ \hline \end{array}$$



Booth's Algorithm

Group in pairs of two
starting from LSB

$$\begin{array}{r} 0 \ 1 \ 0 \ 1 \ 0 \\ * \ 0 \ -1 \ +1 \ 0 \ 0 \ -1 \\ \hline \end{array}$$

Bit Pair Recoding

Original Problem:

$$\begin{array}{r} 0 \ 1 \ 0 \ 1 \ 0 \quad (+10) \\ * \ 1 \ 0 \ 1 \ 1 \ 1 \ 0 \quad (-9) \\ \hline \end{array}$$

Booth's Algorithm

Find pair equivalent
using binary place
values (e.g. $0*2 + (-1)*1 = -1$)

$$\begin{array}{r} 0 \ 1 \ 0 \ 1 \ 0 \\ * \ 0 \ -1 \ +1 \ 0 \ 0 \ -1 \\ \hline \end{array}$$


$\begin{array}{cc} 2 & 1 \\ \downarrow & \downarrow \end{array} \quad \begin{array}{cc} 2 & 1 \\ \downarrow & \downarrow \end{array} \quad \begin{array}{cc} 2 & 1 \\ \downarrow & \downarrow \end{array} \quad \text{Place values}$

$$\begin{array}{r} -1 \quad +2 \quad -1 \\ \hline \end{array}$$

Bit Pair Recoding Example

Bit-Pair Recoded Problem:
 
$$\begin{array}{r} 1 \ 1 \ 1 \ 1 \ 0 \quad (-2) \\ * \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \quad (-6) \\ \hline \end{array}$$



Booth's Algorithm

$$\begin{array}{r} * \ 0 - 1 + 1 - 1 \ 0 \\ \hline \end{array}$$

Bit Pair Recoding Example

Original Problem:

$$\begin{array}{r} 1 \ 1 \ 1 \ 1 \ 0 \quad (-2) \\ * \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \quad (-6) \\ \hline \end{array}$$

Booth's Algorithm

$$\begin{array}{r} 1 \ 1 \ 1 \ 1 \ 0 \\ * \ 0 \ -1 \ +1 \ -1 \ 0 \\ \hline \end{array}$$

Find pair equivalent
using place values
(e.g. $-1*2 + 0*1 = -1$)

$$\begin{array}{r} \begin{array}{cc} 2 & 1 \end{array} \quad \begin{array}{cc} 2 & 1 \end{array} \quad \begin{array}{cc} 2 & 1 \end{array} \quad \text{Place values} \\ \begin{array}{c} \downarrow \\ 0 \end{array} \quad \begin{array}{c} \downarrow \\ -1 \end{array} \quad \begin{array}{c} \downarrow \\ -2 \end{array} \\ \hline \end{array}$$

Bit Pair Recoding Example


Original Problem:

$$\begin{array}{r} 1 \ 1 \ 0 \ 1 \ 0 \quad (-6) \\ * \ 0 \ 1 \ 0 \ 0 \ 1 \ 0 \quad (+9) \\ \hline \end{array}$$

↓ Booth's Algorithm

$$\begin{array}{r} 1 \ 1 \ 0 \ 1 \ 0 \\ * +1 -1 \ 0 +1 -1 \\ \hline \end{array}$$

2 1 2 1 2 1 Place values

 

$$\begin{array}{r} +1 \quad -2 \quad +1 \\ \hline \end{array}$$

